

German University in Cairo  
Faculty of Media Engineering and Technology  
Prof. Dr. Slim Abdennadher  
Dr. Aysha ElSafty

**Introduction to Computer Science, Winter Semester 2017**  
**Practice Assignment 10**

Discussion: 30.12.2017 - 4.1.2018

**Exercise 10-1** To be Discussed in Tutorial

Given the following truth table, where  $P, X,$  and  $Y$  are the input variables and  $S$  and  $C$  are the output variables:

$P$	$X$	$Y$	$S$	$C$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Use the sum-of-products-algorithm to determine the Boolean expressions that correspond to the truth table.

**Exercise 10-2**

Using truth tables, show that:

$$X'Y + Y'Z + XZ' = XY' + YZ' + X'Z$$

**Exercise 10-3**

A circuit should be designed to perform the modulus operation of two numbers consisting of two bits each.

Assume that for any number  $N$ ,  $N\%0 = 3$ .

- How many input and output variables are needed?
- Construct the truth table for this circuit
- Using the sum-of-products method, find the Boolean expressions that correspond to the constructed truth table.

**Exercise 10-4** To be Discussed in Tutorial

Given the following truth tables, find the functionality of the designated circuits.

a)

A	B	C	O1
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

b)

A1	A0	B1	B0	O1	O2	O3
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

**Hint: A1A0 and B1B0 are both two numbers consisting of 2 bits each**

c)

A	B	C	D	O1
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1