

Introduction to Computer Science, Winter Semester 2017
 Practice Assignment 11

Discussion: 30.12.2017 - 04.01.2018

Exercise 11-1 To be Discussed in Tutorial

Simplify the Boolean expressions to a minimum number of literals using the Boolean algebra. Please mention the applied rules.

$x + 0 = x$	$x * 1 = x$	
$x + 1 = 1$	$x * 0 = 0$	
$x + x = x$	$x * x = x$	
$x + x' = 1$	$x * x' = 0$	
$(x')' = x$		
$x + y = y + x$	$xy = yx$	Commutativity
$x + (y + z) = (x + y) + z$	$x(yz) = (xy)z$	Associativity
$x(y + z) = xy + xz$	$x + yz = (x + y)(x + z)$	Distributivity
$(x + y)' = x'y'$	$(xy)' = x' + y'$	DeMorgan's Law

a) $ABC + ABC' + A'B$

Solution:

$$\begin{aligned}
 &ABC + ABC' + A'B \\
 &= AB(C + C') + A'B \quad \text{(Distributivity)} \\
 &= AB * 1 + A'B \quad [x + x' = 1] \\
 &= AB + A'B \quad [x * 1 = x] \\
 &= BA + BA' \quad \text{(Commutativity)} \\
 &= B(A + A') \quad \text{(Distributivity)} \\
 &= B * 1 \quad [x + x' = 1] \\
 &= B \quad [x * 1 = x]
 \end{aligned}$$

b) $(A + B)'(A' + B')$

Solution:

$$\begin{aligned}
 &(A + B)'(A' + B') \\
 &= (A'B')(A' + B') \quad [(x + y)' = x'y'] \\
 &= A'B'A' + A'B'B' \quad \text{(Distributivity)} \\
 &= A'A'B' + A'B'B' \quad \text{(Commutativity)} \\
 &= A'B' + A'B' \quad [x * x = x] \\
 &= A'B' \quad [x + x = x] \\
 &= (A + B)' \quad \text{(DeMorgan's Law)}
 \end{aligned}$$

c) $(A + B' + AB')(AB + A'C + BC)$

Solution:

$$\begin{aligned}
 & (A + B' + AB')(AB + A'C + BC) \\
 &= (A + B'(1 + A))(AB + BC + A'C) && \text{(Distributivity)} \\
 &= (A + B'(A + 1))(AB + BC + A'C) && \text{(Commutativity)} \\
 &= (A + B' * 1)(AB + BC + A'C) && [(x + 1) = 1] \\
 &= (A + B')(AB + BC + A'C) && [(x * 1) = x] \\
 &= (A + B') * AB + (A + B') * BC + (A + B') * A'C && \text{(Distributivity)} \\
 &= AB * (A + B') + BC * (A + B') + A'C * (A + B') && \text{(Commutativity)} \\
 &= ABA + ABB' + BCA + BCB' + A'CA + A'CB' && \text{(Distributivity)} \\
 &= AAB + ABB' + BCA + BB'C + AA'C + A'CB' && \text{(Commutativity)} \\
 &= AB + ABB' + BCA + BB'C + AA'C + A'CB' && [(x * x) = x] \\
 &= AB + 0 + BCA + 0 + 0 + A'CB' && [(x * x') = 0] \\
 &= AB + BCA + A'CB' && [(x + 0) = x] \\
 &= AB + ABC + A'B'C && \text{(Commutativity)} \\
 &= AB(1 + C) + A'B'C && \text{(Distributivity)} \\
 &= AB(C + 1) + A'B'C && \text{(Commutativity)} \\
 &= AB * 1 + A'B'C && [(x + 1) = 1] \\
 &= AB + A'B'C && [(x * 1) = x]
 \end{aligned}$$

d) $P'XY + PX'Y + PXY' + PXY$

Solution:

$$\begin{aligned}
 & P'XY + PX'Y + PXY' + PXY \\
 &= PXY + P'XY + PX'Y + PXY' && \text{(Commutativity)} \\
 &= XYP + XYP' + PX'Y + PXY' && \text{(Commutativity)} \\
 &= XY(P + P') + PX'Y + PXY' && \text{(Distributivity)} \\
 &= XY * 1 + PX'Y + PXY' && [(x + x') = 1] \\
 &= XY + PX'Y + PXY' && [(x * 1) = x] \\
 &= XY + P(X'Y + XY') && \text{(Distributivity)}
 \end{aligned}$$

e) $(AB)'(A + B)$

Solution:

$$\begin{aligned}
 & (AB)'(A + B) \\
 &= (A' + B')(A + B) && [(xy)' = x' + y'] \\
 &= (A' + B')A + (A' + B')B && \text{(Distributivity)} \\
 &= A(A' + B') + B(A' + B') && \text{(Commutativity)} \\
 &= AA' + AB' + BA' + BB' && \text{(Commutativity)} \\
 &= 0 + AB' + BA' + 0 && [(x * x') = 0] \\
 &= AB' + 0 + BA' + 0 && \text{(Commutativity)} \\
 &= AB' + BA' && [(x + 0) = x]
 \end{aligned}$$

To construct a circuit for $(AB)'(A + B)$, we will need 4 gates. To construct a circuit for $AB' + BA'$, we need 5 gates. Thus $(AB)'(A + B)$ is simpler than $AB' + BA'$.

f) $B + A'C + AB'$

Solution:

$$\begin{aligned}
 & B + A'C + AB' \\
 &= B + AB' + A'C && \text{(Commutativity)} \\
 &= B + B'A + A'C && \text{(Commutativity)} \\
 &= (B + B')(B + A) + A'C && [(x + yz) = (x + y)(x + z)] \\
 &= 1 * (B + A) + A'C && [(x + x' = 1)] \\
 &= (B + A) * 1 + A'C && \text{(Commutativity)} \\
 &= (B + A) + A'C && [(x * 1 = x)] \\
 &= A + A'C + B && \text{(Commutativity)} \\
 &= (A + A')(A + C) + B && [(x + yz) = (x + y)(x + z)] \\
 &= 1 * (A + C) + B && [(x + x' = 1)] \\
 &= (A + C) * 1 + B && \text{(Commutativity)} \\
 &= A + C + B && [(x * 1 = x)]
 \end{aligned}$$

g) $AB + A'C + BC$

Solution:

$$\begin{aligned}
 & AB + A'C + BC \\
 &= AB + A'C + BC * 1 && [(x * 1 = x)] \\
 &= AB + A'C + BC(A + A') && [(x + x' = 1)] \\
 &= AB + A'C + BCA + BCA' && \text{(Distributivity)} \\
 &= AB + A'C + ABC + A'CB && \text{(Commutativity)} \\
 &= AB + ABC + A'C + A'CB && \text{(Commutativity)} \\
 &= AB(1 + C) + A'C(1 + B) && \text{(Distributivity)} \\
 &= AB(C + 1) + A'C(B + 1) && \text{(Commutativity)} \\
 &= AB * 1 + A'C * 1 && [(x + 1 = 1)] \\
 &= AB + A'C
 \end{aligned}$$

Exercise 11-2

Given the following Boolean expression, simplify it to a minimum number of literals using the Boolean algebra. Please mention the applied rules.

$$((A + B)(B' + C' + D')) + B'C'(A + B' + C) + A'C + D$$

Hint: The circuit of the simplified expression consists of zero gates.

Solution:


$$\begin{aligned}
&= AB' + AC' + AD' + BB' + BC' + BD' + AB'C' + B'B'C' + B'C'C + A'C + D && \text{(Distributivity)} \\
&= AB' + AC' + BB' + BC' + BD' + AB'C' + B'C' + B'C'C + A'C + D + AD' && \text{(Associativity)} \\
&= AB' + AC' + BB' + BC' + BD' + AB'C' + B'C' + B'C'C + A'C + (D + A)(D + D') && \text{(Distributivity)} \\
&= AB' + AC' + BB' + BC' + BD' + AB'C' + B'C' + B'C'C + A'C + (D + A)(1) && (x + x' = 1) \\
&= AB' + AC' + BB' + BC' + BD' + AB'C' + B'C' + B'C'C + A'C + D + A && (x * 1 = x) \\
&= AB' + AC' + BB' + BD' + AB'C' + B'C'C + A'C + D + A + BC' + B'C' && \text{(Associativity)} \\
&= AB' + AC' + BB' + BD' + AB'C' + B'C'C + A'C + D + A + C'(B + B') && \text{(Distributivity)} \\
&= AB' + AC' + BB' + BD' + AB'C' + B'C'C + A'C + D + A + C'(1) && (x + x' = 1) \\
&= AB' + AC' + BB' + BD' + AB'C' + B'C'C + A'C + D + A + C' && (x * 1 = x) \\
&= AB' + AC' + BB' + BD' + AB'C' + B'C'C + D + A + C' + A'C && \text{(Associativity)} \\
&= AB' + AC' + BB' + BD' + AB'C' + B'C'C + D + A + (C' + A')(C' + C) && \text{(Distributivity)} \\
&= AB' + AC' + BB' + BD' + AB'C' + B'C'C + D + A + (C' + A')(1) && (x + x' = 1) \\
&= AB' + AC' + BB' + BD' + AB'C' + B'C'C + D + A + C' + A' && (x * 1 = x) \\
&= AB' + AC' + BB' + BD' + AB'C' + B'C'C + D + C' + (A + A') && \text{(Associativity)} \\
&= AB' + AC' + BB' + BD' + AB'C' + B'C'C + D + C' + 1 && (x + x' = 1) \\
&= (AB' + AC' + BB' + BD' + AB'C' + B'C'C + D + C') + 1 && (x + 1 = 1) \\
&= 1
\end{aligned}$$

Exercise 11-3

Use AND, OR and NOT gates to implement the circuits represented by the following two expressions:

$$\begin{aligned}
S &= P'X'Y + P'XY' + PX'Y' + PXY \\
C &= P'XY + PX'Y + PXY' + PXY
\end{aligned}$$

Solution:

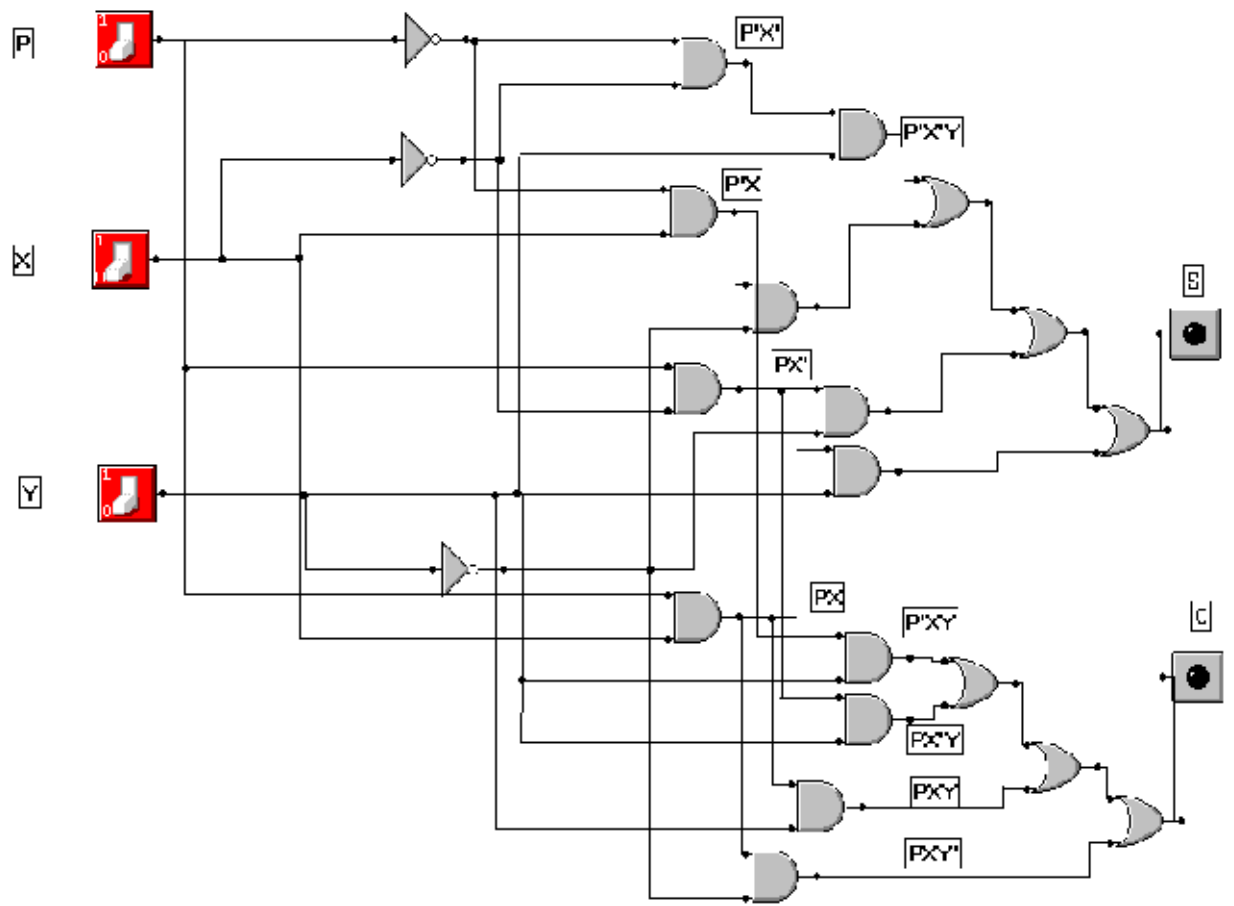


Exercise 11-4 To be Discussed in Tutorial

Draw a logic circuit that corresponds to each of the expressions shown below:


a) $AB' + A'C'D' + A'B'D + A'B'CD'$

Solution:

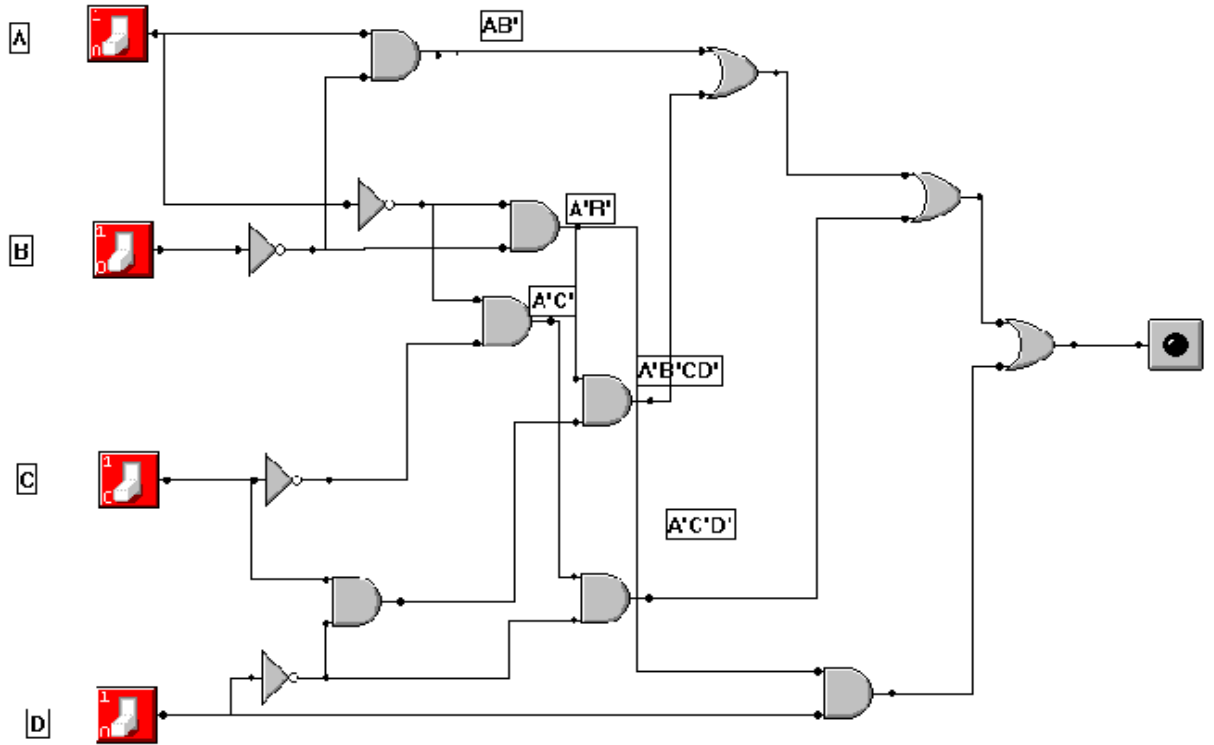


b) $B' + A'C'D'$

Solution:

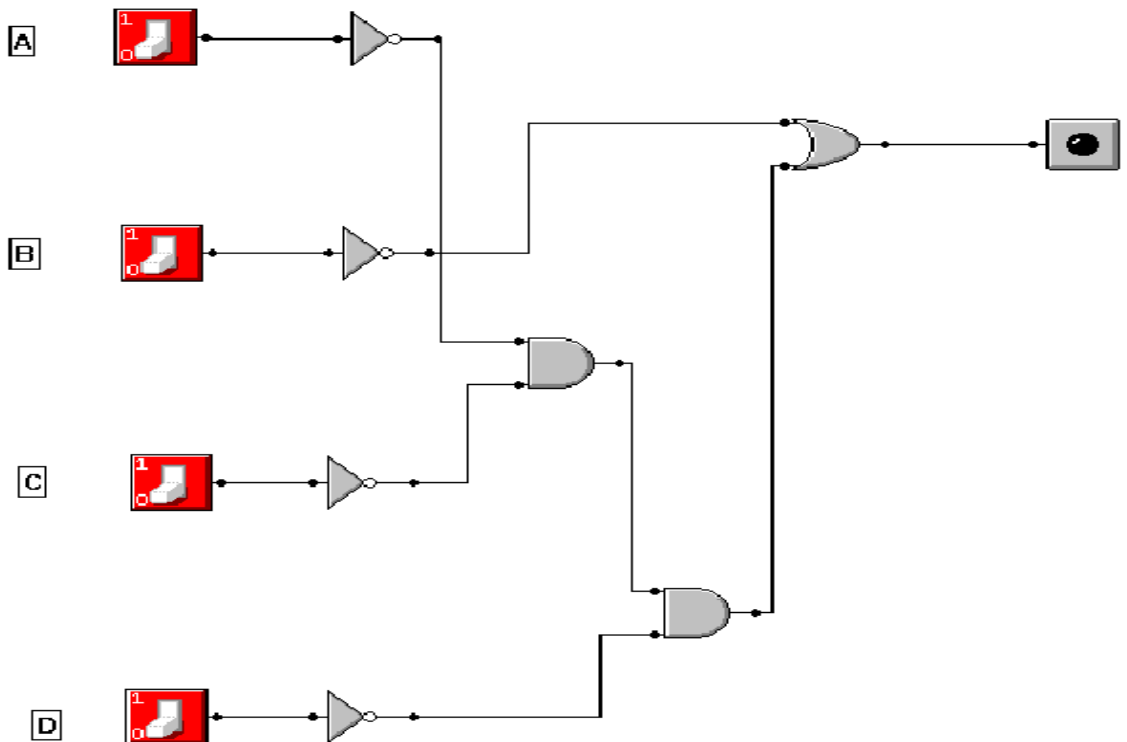

c) $(A' + B' + C + D')(A + B + C' + D)$

Solution:

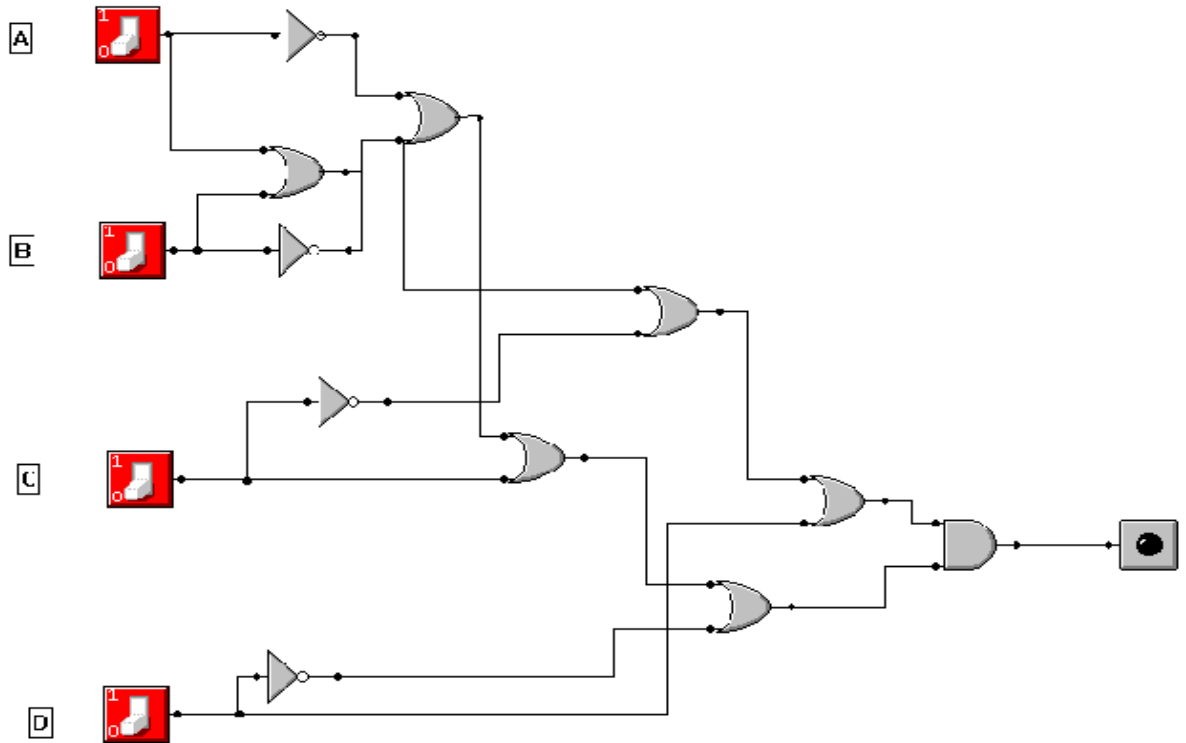

Exercise 11-5

Given the following the following truth table, where **A**, **B** and **C** are the input variables and **X** is the output variable.

A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

- a) Use the sum-of-products algorithm to find the Boolean expression that describes the output of the truth table.

Solution:

$$x = A'B'C' + A'BC + AB'C + ABC'$$


- b) What is the functionality of the circuit?

Solution:

The circuit computes the parity of a number. The parity bit is equal to 1 if the number of ones is even otherwise, the parity bit is equal to 0.

c) Draw the Boolean circuit. **Note** that each gate can have only two inputs.

Solution:

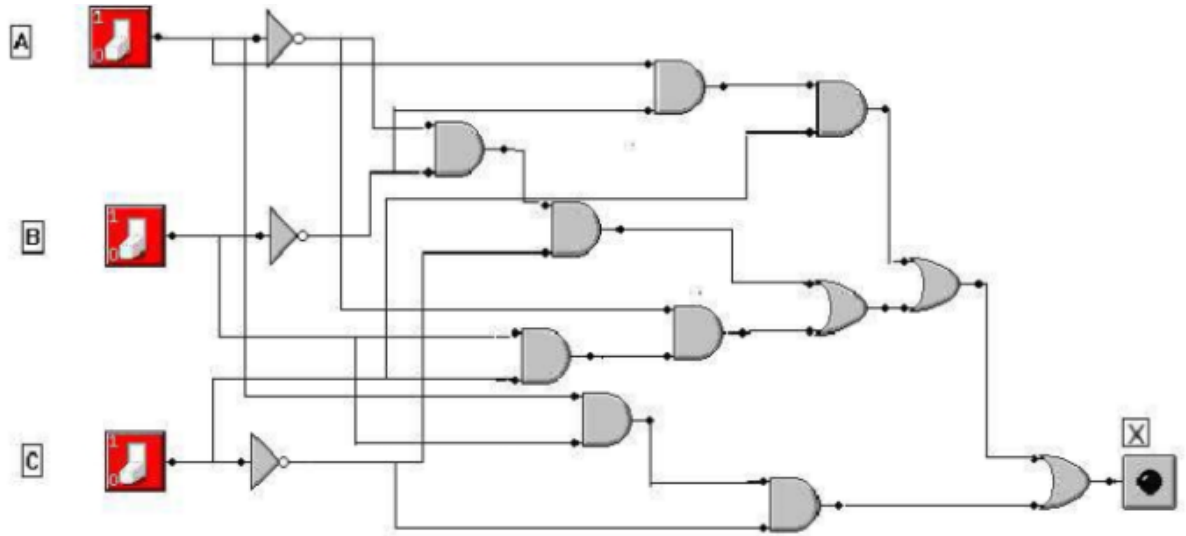

Exercise 11-6 To be Discussed in Tutorial
Comparator

A one-bit comparator is a circuit that takes two numbers consisting of one bit each and outputs 1 if the numbers are equal, 0 otherwise.

a) Construct a truth table for a one bit equality comparator.

Solution:


x	y	Output
0	0	1
0	1	0
1	0	0
1	1	1

b) Assume that you have already manufactured one-bit comparators.




Design a circuit that uses one-bit comparators and AND-gates to check the equality of two numbers consisting of 4 bits each.

Solution:

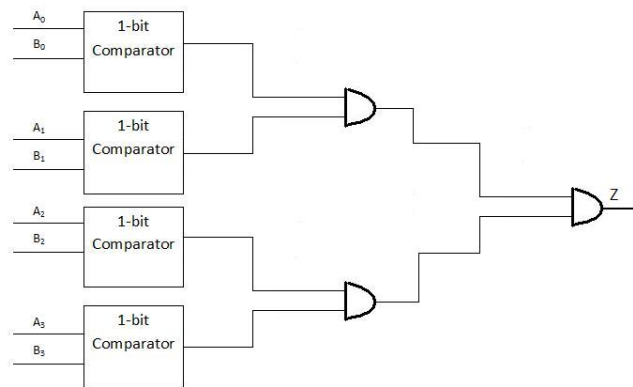


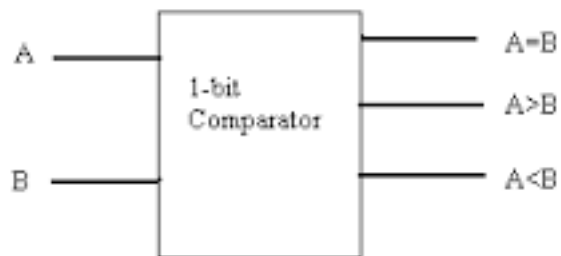- c) Assume that our one-bit comparator was modified to have two input variables A, B and three output variables (one checking for $A = B$, one checking for $A > B$ and one checking for $A < B$).



Design a circuit that uses the modified one-bit comparators with other gates to compare two numbers consisting of 2 bits each. **Do not draw the truth table.**

Solution:

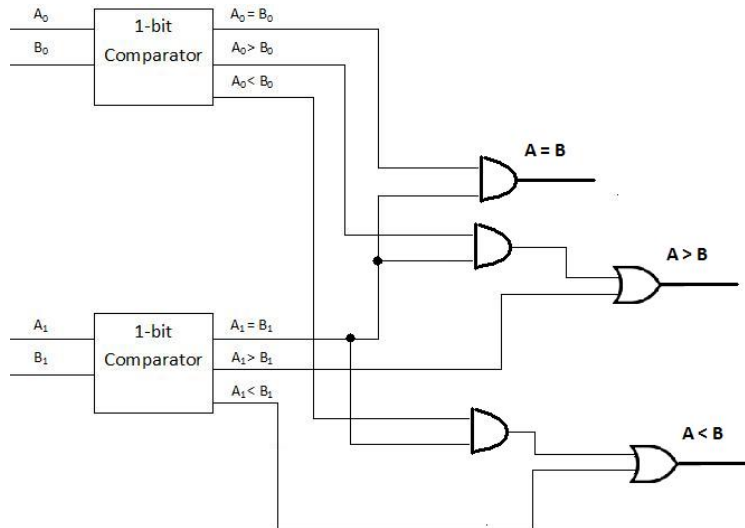

Exercise 11-7 To be Discussed in Tutorial

A circuit should be designed to perform the operation $(A - 1)$ where A represents a number in sign/magnitude notation consisting of 2 bits.

- a) How many output variables are needed? Justify your answer.

Solution:

3 output variables are needed. 2 bits in sign magnitude can represent a range of $[-1, 1]$. Thus the output of calculating $-1 - 1$, which is equal to -2 , needs 3 bits to represent it in sign/magnitude notation (110).

- b) Construct the truth table for this circuit.

Solution:

A1	A2	O1	O2	O3
0	0	1	0	1
0	1	0	0	0
1	0	1	0	1
1	1	1	1	0

- c) Use the sum-of-products algorithm to find the Boolean expressions that corresponds to the truth table.

Solution:

$$O1 = A1'A2' + A1A2' + A1A2$$

$$O2 = A1A2$$

$$O3 = A1'A2' + A1A2'$$

- d) Simplify the Boolean expressions that you got in c) to a minimum number of literals using the Boolean algebra. Please mention the applied rules.

Solution:

$$\begin{aligned}
O1 &= A1'A2' + A1A2' + A1A2 \\
O1 &= A2'A1' + A2'A1 + A1A2 \quad (\text{Commutativity}) \\
O1 &= A2'(A1' + A1) + A1A2 \quad (\text{Distributivity}) \\
O1 &= A2' * 1 + A1A2 \quad (x' + x = 1) \\
O1 &= A2' + A1A2 \quad (x * 1 = x) \\
O1 &= (A2' + A1)(A2' + A2) \quad (\text{Distributivity}) \\
O1 &= (A2' + A1) * 1 \quad (x' + x = 1) \\
O1 &= (A2' + A1) \quad (x * 1 = x) \\
\\
O2 &= A1A2 \\
\\
O3 &= A1'A2' + A1A2' \\
O3 &= A2'A1' + A2'A1 \quad (\text{Commutativity}) \\
O3 &= A2'(A1' + A1) \quad (\text{Distributivity}) \\
O3 &= A2' * 1 \quad (x' + x = 1) \\
O3 &= A2' \quad (x * 1 = x)
\end{aligned}$$

e) Draw a logic circuit that corresponds to the simplified expressions you got in d).

Solution:

