

Introduction to Computer Science, Winter Semester 2018
 Practice Assignment 10

Discussion: 29.12.2018 - 03.01.2018

Exercise 10-1

Given the following truth table, where **A**, **B** and **C** are the input variables and **X** is the output variable

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

- a) Use the sum-of-products algorithm to find the Boolean expression that describes the output of the truth table.

Solution:

$$X = AB'C' + AB'C + ABC' + ABC$$

- b) What is the functionality of the circuit? you should express it in form of an arithmetic operation.


Solution:

Assuming that input variables correspond to a decimal number N from 0 to 7, the circuit will perform an integer division $X = N / 4$ it could also be described as a logical operation $N \geq 4$

- c) Draw the Boolean circuit.

Note: each gate can have only two inputs.

Solution:

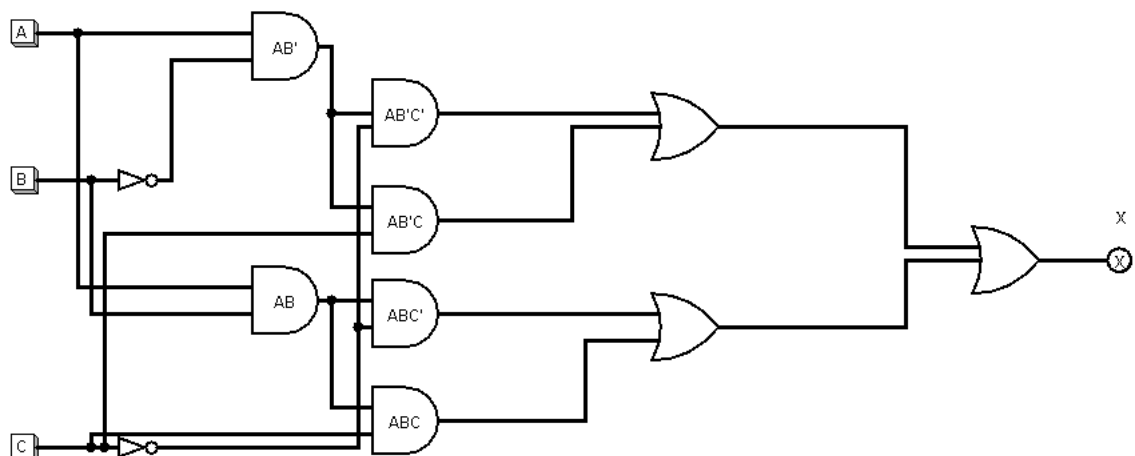

d) Simplify the Boolean expression using the Boolean algebra. Specify the applied rules.

$x + 0 = x$	$x * 1 = x$	
$x + 1 = 1$	$x * 0 = 0$	
$x + x = x$	$x * x = x$	
$x + x' = 1$	$x * x' = 0$	
$(x')' = x$		
$x + y = y + x$	$xy = yx$	Commutativity
$x + (y + z) = (x + y) + z$	$x(yz) = (xy)z$	Associativity
$x(y + z) = xy + xz$	$x + yz = (x + y)(x + z)$	Distributivity
$(x + y)' = x'y'$	$(xy)' = x' + y'$	DeMorgan's Law

Solution:

$$AB'C' + AB'C + ABC' + ABC$$

$$AB'C' + AB'C + AB(C' + C)$$

(Distributivity)

$$AB'C' + AB'C + AB * 1$$

$$(x + x' = 1)$$

$$AB'C' + AB'C + AB$$

$$(x * 1 = x)$$

$$AB'(C' + C) + AB$$

(Distributivity)

$$AB' * 1 + AB$$

$$(x + x' = 1)$$

$$AB' + AB$$

$$(x * 1 = x)$$

$$A(B' + B)$$

(Distributivity)


$$A * 1$$

$$(x + x' = 1)$$

$$A$$

Exercise 10-2

Given the following circuit

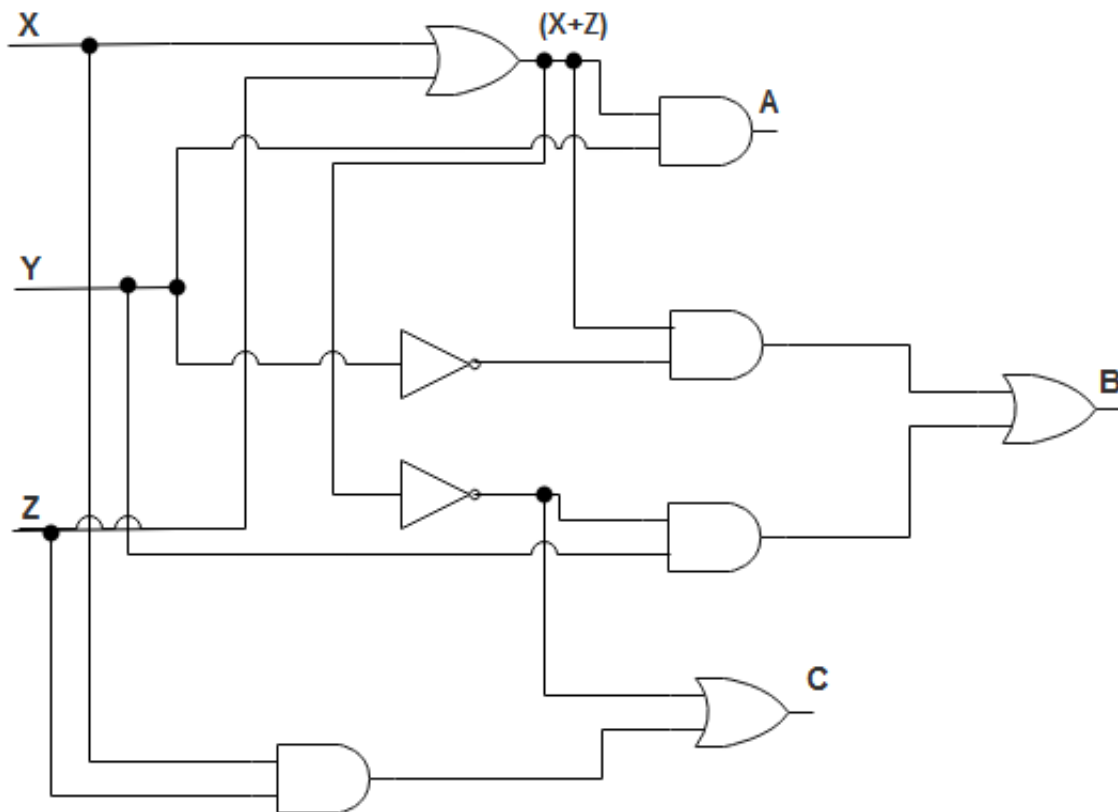

a) Extract the three Boolean expressions for A, B and C from the circuit.

Solution:

$$\begin{aligned} A &= y(x + z) \\ B &= y(x + z)' + y'(x + z) \\ C &= xz + (x + z)' \end{aligned}$$

b) Draw a truth table for the circuit.

Solution:

X	Y	Z	A	B	C
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	1	1
1	1	0	1	0	0
1	1	1	1	0	1

c) Use the sum-of-products algorithm to determine the Boolean expressions that correspond to the truth table.

Solution:

$$\begin{aligned} A &= x'yz + xyz' + xyz \\ B &= x'y'z + x'yz' + xy'z' + xy'z \\ C &= x'y'z' + x'yz' + xy'z + xyz \end{aligned}$$

d) Simplify the Boolean expressions received from part (c) to reach the expressions in part (a). Use the axioms of the Boolean Algebra. Please mention the applied rules.

$x + 0 = x$	$x * 1 = x$	
$x + 1 = 1$	$x * 0 = 0$	
$x + x = x$	$x * x = x$	
$x + x' = 1$	$x * x' = 0$	
$(x')' = x$		
$x + y = y + x$	$xy = yx$	Commutativity
$x + (y + z) = (x + y) + z$	$x(yz) = (xy)z$	Associativity
$x(y + z) = xy + xz$	$x + yz = (x + y)(x + z)$	Distributivity
$(x + y)' = x'y'$	$(xy)' = x' + y'$	DeMorgan's Law

Solution:

- $A = x'yz + xyz' + xyz$
 $= x'yz + xy(z' + z)$ (Distributivity)
 $= x'yz + xy$ ($x + x' = 1$)
 $= yx'z + yx$ (Commutativity)
 $= y(x'z + x)$ (Distributivity)
 $= y((x' + x)(z + x))$ (Distributivity)
 $= y(z + x)$ ($x + x' = 1$)
- $B = x'y'z + x'yz' + xy'z' + xy'z$
 $= x'y'z + x'yz' + xy'(z' + z)$ (Distributivity)
 $= x'y'z + x'yz' + xy'$ ($x + x' = 1$)
 $= x'y'z + xy' + x'yz'$ (Commutativity)
 $= y'x'z + y'x + x'yz'$ (Commutativity)
 $= y'(x'z + x) + x'yz'$ (Distributivity)

$$\begin{aligned}
&= y'((x' + x)(z + x)) + x'yz' && \text{(Distributivity)} \\
&= y'(z + x) + x'yz' && (x + x' = 1) \\
&= y'(z + x) + yx'z' && \text{(Commutativity)} \\
&= y(z + x) + y(x + z)' && \text{(DeMorgan's Law)}
\end{aligned}$$

- $C = x'y'z' + x'yz' + xy'z + xyz$
- $= x'z'y' + x'z'y + xzy' + xzy$ && (Commutativity)
- $= x'z'(y' + y) + xz(y' + y)$ && (Distributivity)
- $= x'z' + xz$ && ($x + x' = 1$)
- $= (x + z)' + xz$ && (DeMorgan's Law)

Exercise 10-3

Given the following truth table, where $P, X,$ and Y are the input variables and S and C are the output variables:

P	X	Y	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- a) Use the sum-of-products-algorithm to determine the boolean expressions that correspond to the truth table.

Solution:

- a) Using the sum-of-products-algorithm

$$\begin{aligned}
S &= P'X'Y + P'XY' + PX'Y' + PXY \\
C &= P'XY + PX'Y + PXY' + PXY
\end{aligned}$$

Exercise 10-4

Using truth tables, show that:

$$X'Y + Y'Z + XZ' = XY' + YZ' + X'Z$$

Solution:

- Truth table for $X'Y + Y'Z + XZ'$

X	Y	Z	$X'Y$	$Y'Z$	XZ'	$X'Y + Y'Z + XZ'$
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	1	0	0	1
0	1	1	1	0	0	1
1	0	0	0	0	1	1
1	0	1	0	1	0	1
1	1	0	0	0	1	1
1	1	1	0	0	0	0

- Truth table for $XY' + YZ' + X'Z$

X	Y	Z	XY'	YZ'	$X'Z$	$XY' + YZ' + X'Z$
0	0	0	0	0	0	0
0	0	1	0	0	1	1
0	1	0	0	1	0	1
0	1	1	0	0	1	1
1	0	0	1	0	0	1
1	0	1	1	0	0	1
1	1	0	0	1	0	1
1	1	1	0	0	0	0

Exercise 10-5

A circuit should be designed to perform the operation $(A - 1)$ where A represents a number in sign/magnitude notation consisting of 2 bits.

- a) How many output variables are needed? Justify your answer.

Solution:

3 output variables are needed. 2 bits in sign magnitude can represent a range of $[-1, 1]$. Thus the output of calculating $-1 - 1$, which is equal to -2 , needs 3 bits to represent it in sign/magnitude notation (110).

- b) Construct the truth table for this circuit.

Solution:

A1	A2	O1	O2	O3
0	0	1	0	1
0	1	0	0	0
1	0	1	0	1
1	1	1	1	0

- c) Use the sum-of-products algorithm to find the boolean expressions that corresponds to the truth table.

Solution:

$$O1 = A1'A2' + A1A2' + A1A2$$

$$O2 = A1A2$$

$$O3 = A1'A2' + A1A2'$$

Exercise 10-6

A circuit should be designed to perform the modulus operation of two numbers consisting of two bits each.

Assume that for any number N , $N\%0 = 3$.

- a) How many input and output variables are needed?

Solution:

Four input variables and two output variables are needed.

b) Construct the truth table for this circuit

Solution:

A	B	C	D	O1	O2
0	0	0	0	1	1
0	0	0	1	0	0
0	0	1	0	0	0
0	0	1	1	0	0
0	1	0	0	1	1
0	1	0	1	0	0
0	1	1	0	0	1
0	1	1	1	0	1
1	0	0	0	1	1
1	0	0	1	0	0
1	0	1	0	0	0
1	0	1	1	1	0
1	1	0	0	1	1
1	1	0	1	0	0
1	1	1	0	0	1
1	1	1	1	0	0

c) Using the sum-of-products method, find the Boolean expressions that correspond to the constructed truth table.

Solution:

$$O1 = A'B'C'D' + A'BC'D' + AB'C'D' + AB'CD + ABC'D'$$

$$O2 = A'B'C'D' + A'BC'D' + A'BCD' + A'BCD + AB'C'D' + ABC'D' + ABCD'$$

Exercise 10-7

Simplify the Boolean expressions to a minimum number of literals using the Boolean algebra. Please mention the applied rules.

- $ABC + ABC' + A'B$

Solution:

$$\begin{aligned}
 &ABC + ABC' + A'B \\
 = &AB(C + C') + A'B && \text{(Distributivity)} \\
 = &AB * 1 + A'B && [x + x' = 1] \\
 = &AB + A'B && [x * 1 = x] \\
 = &BA + BA' && \text{(Commutativity)} \\
 = &B(A + A') && \text{(Distributivity)} \\
 = &B * 1 && [x + x' = 1] \\
 = &B && [x * 1 = x]
 \end{aligned}$$

- $(A + B)'(A' + B')$

Solution:

$$\begin{aligned}
(A+B)'(A'+B') &= (A'B')(A'+B') \quad [(x+y)' = x'y'] \\
&= A'B'A' + A'B'B' \quad \text{(Distributivity)} \\
&= A'A'B' + A'B'B' \quad \text{(Commutativity)} \\
&= A'B' + A'B' \quad [x*x = x] \\
&= A'B' \quad [x+x = x] \\
&= (A+B)' \quad \text{(DeMorgan's Law)}
\end{aligned}$$

• $(A+B'+AB')(AB+A'C+BC)$

Solution:

$$\begin{aligned}
&(A+B'+AB')(AB+A'C+BC) \\
&= (A+B'(1+A))(AB+BC+A'C) \quad \text{(Distributivity)} \\
&= (A+B'(A+1))(AB+BC+A'C) \quad \text{(Commutativity)} \\
&= (A+B'*1)(AB+BC+A'C) \quad [(x+1) = 1] \\
&= (A+B')(AB+BC+A'C) \quad [(x*1) = x] \\
&= (A+B')*AB + (A+B')*BC + (A+B')*A'C \quad \text{(Distributivity)} \\
&= AB*(A+B') + BC*(A+B') + A'C*(A+B') \quad \text{(Commutativity)} \\
&= ABA + ABB' + BCA + BCB' + A'CA + A'CB' \quad \text{(Distributivity)} \\
&= AAB + ABB' + BCA + BB'C + AA'C + A'CB' \quad \text{(Commutativity)} \\
&= AB + ABB' + BCA + BB'C + AA'C + A'CB' \quad [(x*x) = x] \\
&= AB + 0 + BCA + 0 + 0 + A'CB' \quad [(x*x') = 0] \\
&= AB + BCA + A'CB' \quad [(x+0) = x] \\
&= AB + ABC + A'B'C \quad \text{(Commutativity)} \\
&= AB(1+C) + A'B'C \quad \text{(Distributivity)} \\
&= AB(C+1) + A'B'C \quad \text{(Commutativity)} \\
&= AB*1 + A'B'C \quad [(x+1) = 1] \\
&= AB + A'B'C \quad [(x*1) = x]
\end{aligned}$$

• $P'XY + PX'Y + PXY' + PXY$

Solution:

$$\begin{aligned}
&P'XY + PX'Y + PXY' + PXY \\
&= PXY + P'XY + PX'Y + PXY' \quad \text{(Commutativity)} \\
&= XYP + XYP' + PX'Y + PXY' \quad \text{(Commutativity)} \\
&= XY(P+P') + PX'Y + PXY' \quad \text{(Distributivity)} \\
&= XY*1 + PX'Y + PXY' \quad [(x+x') = 1] \\
&= XY + PX'Y + PXY' \quad [(x*1) = x] \\
&= XY + P(X'Y + XY') \quad \text{(Distributivity)}
\end{aligned}$$

• $(AB)'(A+B)$

Solution:

$$\begin{aligned}
& (AB)'(A+B) \\
&= (A'+B')(A+B) \quad [(xy)' = x' + y'] \\
&= (A'+B')A + (A'+B')B \quad \text{(Distributivity)} \\
&= A(A'+B') + B(A'+B') \quad \text{(Commutativity)} \\
&= AA' + AB' + BA' + BB' \quad \text{(Commutativity)} \\
&= 0 + AB' + BA' + 0 \quad [(x * x' = 0)] \\
&= AB' + 0 + BA' + 0 \quad \text{(Commutativity)} \\
&= AB' + BA' \quad [(x + 0 = x)]
\end{aligned}$$

To construct a circuit for $(AB)'(A+B)$, we will need 4 gates. To construct a circuit for $AB' + BA'$, we need 5 gates. Thus $(AB)'(A+B)$ is simpler than $AB' + BA'$.

- $B + A'C + AB'$

Solution:

$$\begin{aligned}
& B + A'C + AB' \\
&= B + AB' + A'C \quad \text{(Commutativity)} \\
&= B + B'A + A'C \quad \text{(Commutativity)} \\
&= (B + B')(B + A) + A'C \quad [(x + yz) = (x + y)(x + z)] \\
&= 1 * (B + A) + A'C \quad [(x + x' = 1)] \\
&= (B + A) * 1 + A'C \quad \text{(Commutativity)} \\
&= (B + A) + A'C \quad [(x * 1 = x)] \\
&= A + A'C + B \quad \text{(Commutativity)} \\
&= (A + A')(A + C) + B \quad [(x + yz) = (x + y)(x + z)] \\
&= 1 * (A + C) + B \quad [(x + x' = 1)] \\
&= (A + C) * 1 + B \quad \text{(Commutativity)} \\
&= A + C + B \quad [(x * 1 = x)]
\end{aligned}$$

- $AB + A'C + BC$

Solution:

$$\begin{aligned}
& AB + A'C + BC \\
&= AB + A'C + BC * 1 \quad [(x * 1 = x)] \\
&= AB + A'C + BC(A + A') \quad [(x + x' = 1)] \\
&= AB + A'C + BCA + BCA' \quad \text{(Distributivity)} \\
&= AB + A'C + ABC + A'CB \quad \text{(Commutativity)} \\
&= AB + ABC + A'C + A'CB \quad \text{(Commutativity)} \\
&= AB(1 + C) + A'C(1 + B) \quad \text{(Distributivity)} \\
&= AB(C + 1) + A'C(B + 1) \quad \text{(Commutativity)} \\
&= AB * 1 + A'C * 1 \quad [(x + 1 = 1)] \\
&= AB + A'C
\end{aligned}$$

Exercise 10-8

Given the following Boolean expression, simplify it to a minimum number of literals using the Boolean algebra. Please mention the applied rules.

$$((A + B)(B' + C' + D')) + B'C'(A + B' + C) + A'C + D$$

Hint: The circuit of the simplified expression consists of zero gates.

Solution:


$$\begin{aligned}
 &= AB' + AC' + AD' + BB' + BC' + BD' + AB'C' + B'B'C' + B'C'C + A'C + D && \text{(Distributivity)} \\
 &= AB' + AC' + BB' + BC' + BD' + AB'C' + B'C' + B'C'C + A'C + D + AD' && \text{(Associativity)} \\
 &= AB' + AC' + BB' + BC' + BD' + AB'C' + B'C' + B'C'C + A'C + (D + A)(D + D') && \text{(Distributivity)} \\
 &= AB' + AC' + BB' + BC' + BD' + AB'C' + B'C' + B'C'C + A'C + (D + A)(1) && (x + x' = 1) \\
 &= AB' + AC' + BB' + BC' + BD' + AB'C' + B'C' + B'C'C + A'C + D + A && (x * 1 = x) \\
 &= AB' + AC' + BB' + BD' + AB'C' + B'C'C + A'C + D + A + BC' + B'C' && \text{(Associativity)} \\
 &= AB' + AC' + BB' + BD' + AB'C' + B'C'C + A'C + D + A + C'(B + B') && \text{(Distributivity)} \\
 &= AB' + AC' + BB' + BD' + AB'C' + B'C'C + A'C + D + A + C'(1) && (x + x' = 1) \\
 &= AB' + AC' + BB' + BD' + AB'C' + B'C'C + A'C + D + A + C' && (x * 1 = x) \\
 &= AB' + AC' + BB' + BD' + AB'C' + B'C'C + D + A + C' + A'C && \text{(Associativity)} \\
 &= AB' + AC' + BB' + BD' + AB'C' + B'C'C + D + A + (C' + A')(C' + C) && \text{(Distributivity)} \\
 &= AB' + AC' + BB' + BD' + AB'C' + B'C'C + D + A + (C' + A')(1) && (x + x' = 1) \\
 &= AB' + AC' + BB' + BD' + AB'C' + B'C'C + D + A + C' + A' && (x * 1 = x) \\
 &= AB' + AC' + BB' + BD' + AB'C' + B'C'C + D + C' + (A + A') && \text{(Associativity)} \\
 &= AB' + AC' + BB' + BD' + AB'C' + B'C'C + D + C' + 1 && (x + x' = 1) \\
 &= (AB' + AC' + BB' + BD' + AB'C' + B'C'C + D + C') + 1 && (x + 1 = 1) \\
 &= 1
 \end{aligned}$$

Exercise 10-9

Use AND, OR and NOT gates to implement the circuits represented by the following two expressions:

$$\begin{aligned}
 S &= P'X'Y + P'XY' + PX'Y' + PXY \\
 C &= P'XY + PX'Y + PXY' + PXY
 \end{aligned}$$

Solution:

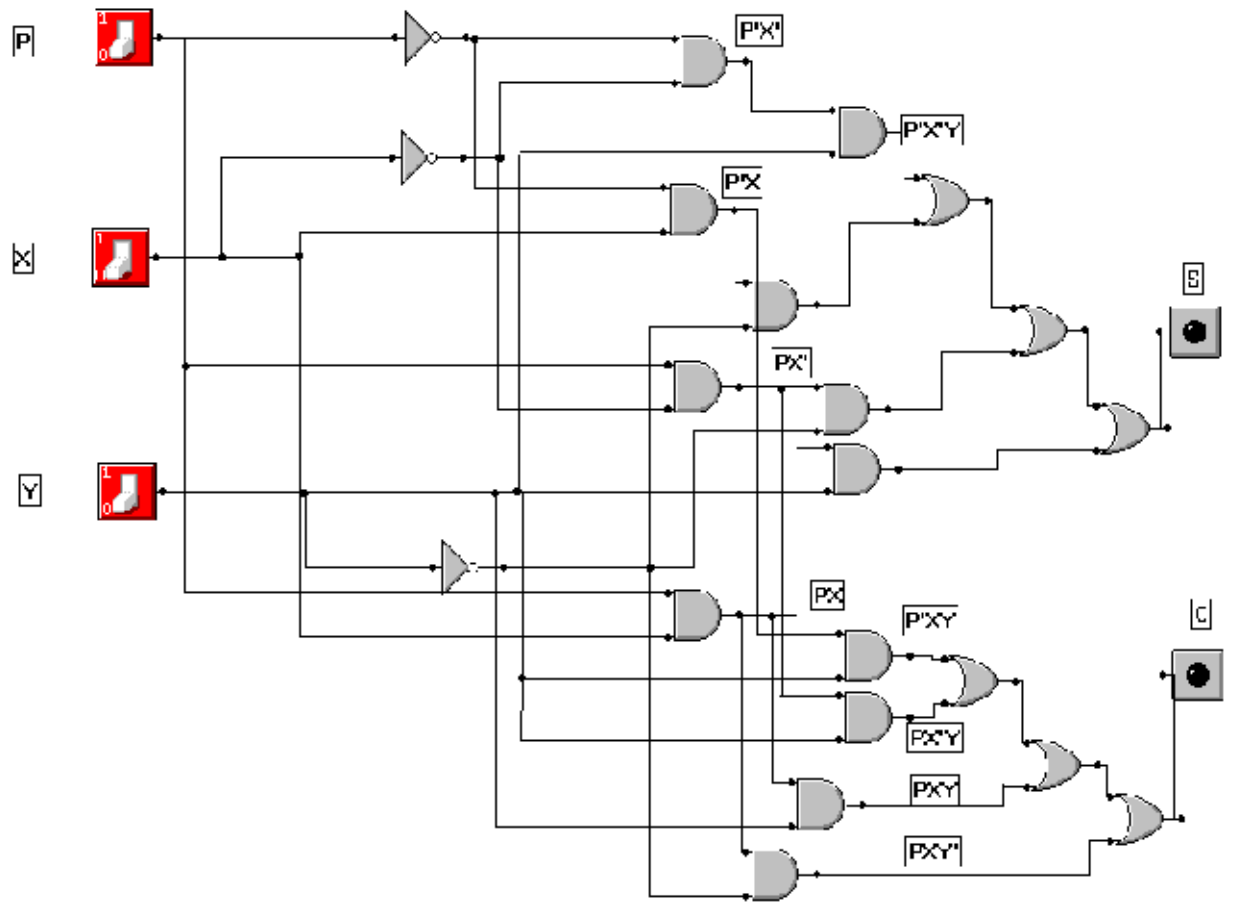


Exercise 10-10

Draw a logic circuit that corresponds to each of the expressions shown below:


a) $AB' + A'C'D' + A'B'D + A'B'CD'$

Solution:

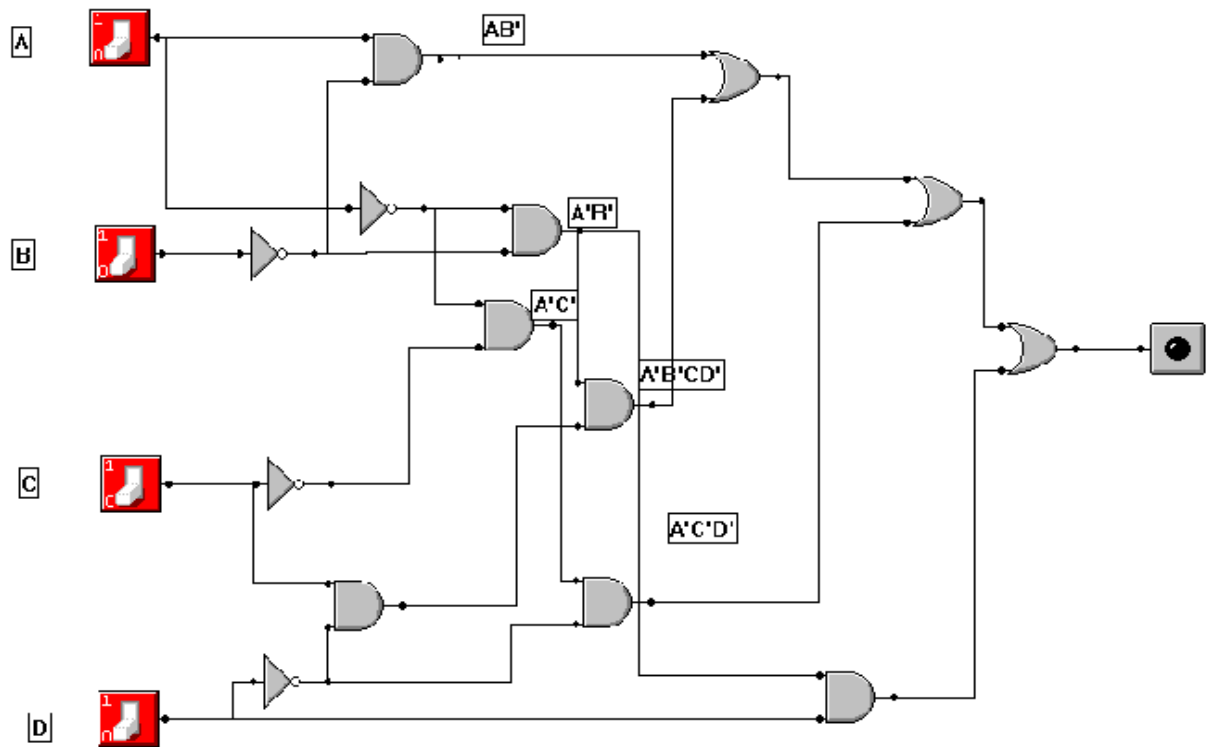


b) $B' + A'C'D'$

Solution:

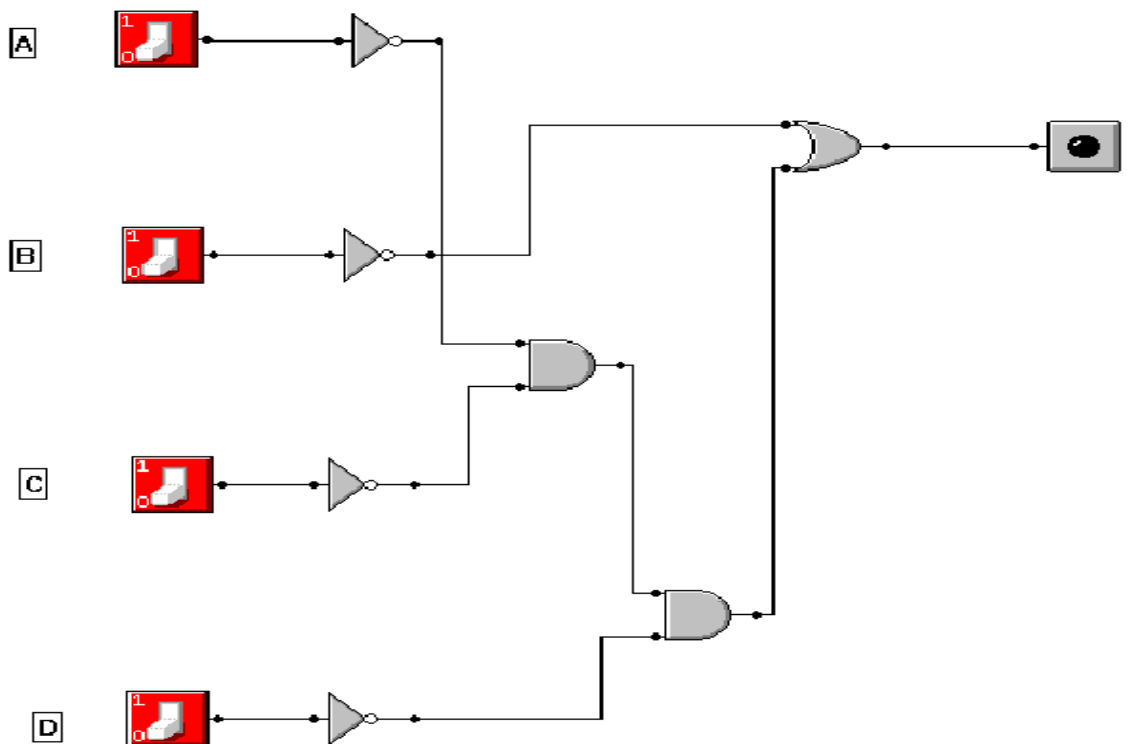

c) $(A' + B' + C + D')(A + B + C' + D)$

Solution:

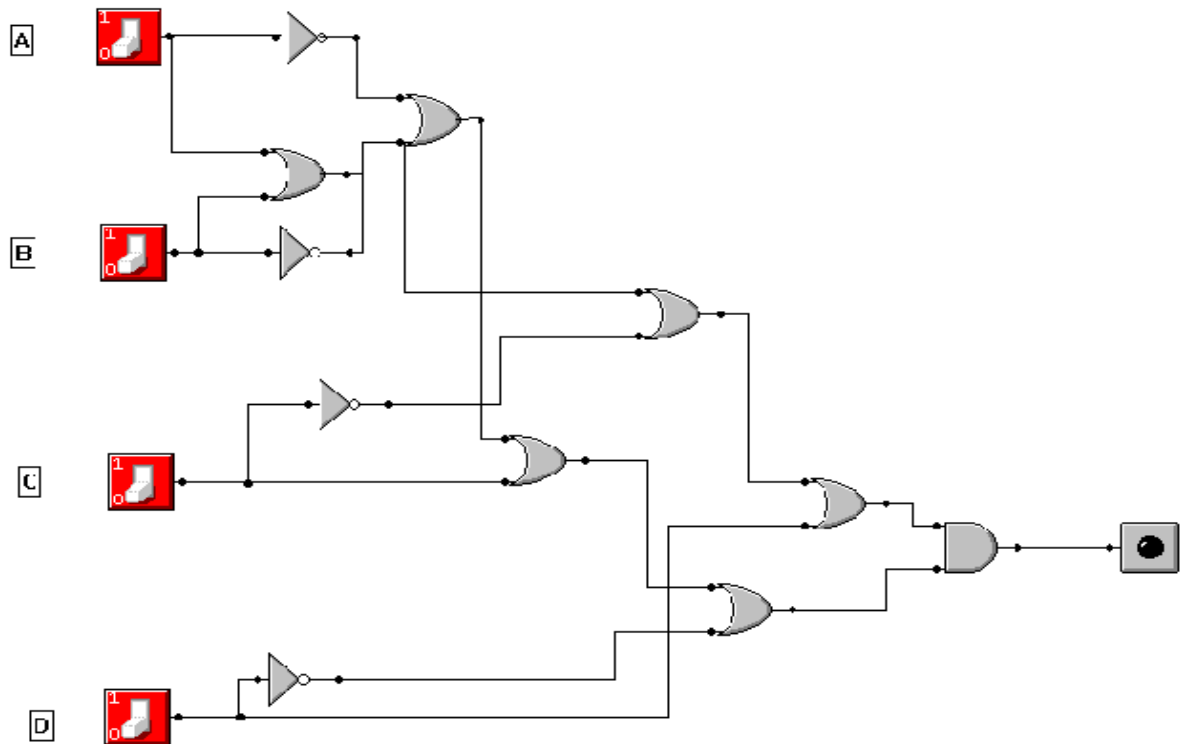

Exercise 10-11

Given the following the following truth table, where **A**, **B** and **C** are the input variables and **X** is the output variable.

A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

- a) Use the sum-of-products algorithm to find the Boolean expression that describes the output of the truth table.

Solution:

$$x = A'B'C' + A'BC + AB'C + ABC'$$

- b) What is the functionality of the circuit?

Solution:

The circuit computes the parity of a number. The parity bit is equal to 1 if the number of ones is even otherwise, the parity bit is equal to 0.

- c) Draw the Boolean circuit. **Note** that each gate can have only two inputs.

Solution:

